

Laboratory Exercise 6

Finite State Machines

Revision of October 30, 2023

In this lab, you will learn how to write Finite State Machines (FSMs) in Verilog and how to use an FSM to control the sequencing of logical operations.

For Parts I and II, you are provided code templates. This provides you with some good examples to use as models for your own code, but they also allow you to focus on the key elements relevant to building the required control sequences without having to write the supporting infrastructure. The amount of code you need to write in these parts is relatively small. Most likely, more of your time will be spent understanding all of the code presented to you and how to modify it. Learning to read other code is also a good thing to learn as you will do that a lot in industry. A good way to start is to reverse engineer a schematic from the code.

1 Part I

In this part you will implement a basic finite state machine (FSM) in Verilog. All FSMs you write in Verilog should follow this structure or you can get into lots of trouble.

You must implement a FSM with an input w and an output z , that recognizes two specific sequences of inputs. When $w = 1$ for four consecutive clock pulses, or when the sequence 1101 appears on w across four consecutive clock cycles, the value of z has to be 1; otherwise, $z = 0$. Overlapping sequences are allowed, so that if $w = 1$ for five consecutive clock cycles the output z will be equal to 1 after the fourth and fifth cycles. Figure 1 illustrates the required relationship between w and z for an example input sequence. A state diagram for this FSM is shown in Figure 2.

Listing 1 shows a partial Verilog file for the FSM. It is the template code in `part1_template.v` that you will need to complete for this part. Study and understand this code as it provides a model for how to clearly describe a finite state machine that will both simulate and run on the FPGA properly.

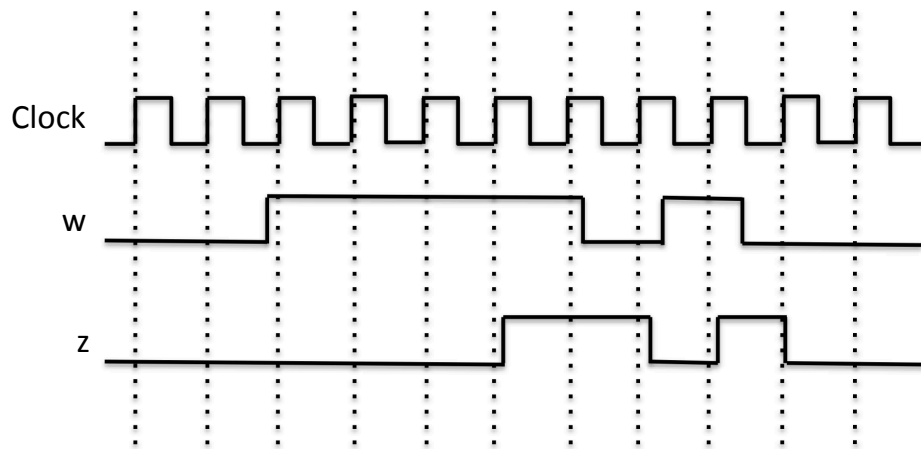


Figure 1: Required timing for the output z .

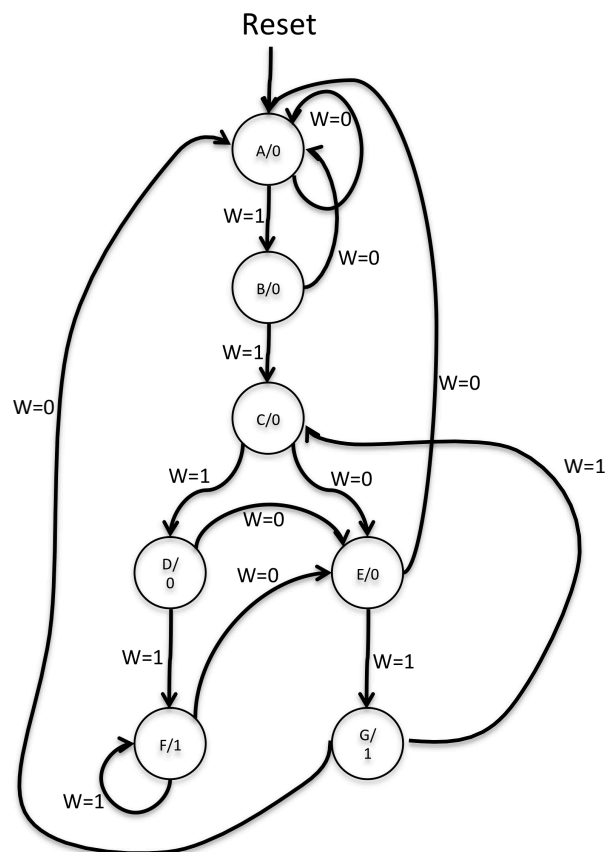


Figure 2: A state diagram for the FSM.

```

module part1(
    input Clock,
    input Reset,
    input w,
    output z,
    output [3:0] CurState
);
    reg [3:0] y_Q, Y_D;
    localparam A=4'd0, B=4'd1, C=4'd2, D=4'd3, E=4'd4, F=4'd5,
        G=4'd6;

    //State table
    always@(*) begin
        case (y_Q)
            A: begin
                if (!w) Y_D = A;
                else Y_D = B;
            end
            B: // Complete
            C: // Complete
            D: // Complete
            E: // Complete
            F: // Complete
            G: // Complete
            default: // Complete
        endcase
    end // state_table

    // State Registers
    always @(posedge Clock) begin
        if(Reset == 1'b1)
            // Should set reset state to state A
        else
            y_Q <= Y_D;
        end // state flip flops

        assign z = ((y_Q == F) | (y_Q == G)); // Output logic

        assign CurState = y_Q;
    endmodule

```

Listing 1: Code template for FSM in part 1

1.1 What to Do

Perform the following steps:

1. Begin with the template code provided online in `part1_template.v`.
2. Complete the state table and the output logic.
3. Simulate your `part1` module with ModelSim to satisfy yourself that your circuit is working. When you are satisfied with your simulations, you can submit to the Automarker.

1.2 Running on FPGA

To run your design on an FPGA, use the mapping shown in Table 1.

<code>part1</code> Port Name	Direction	DE1-SoC Pin Name
<code>Clock</code>	Input	KEY[0]
<code>Reset</code>	Input	SW[0]
<code>w</code>	Input	SW[1]
<code>z</code>	Output	LEDR[9]
<code>CurState</code>	Output	LEDR[3:0] & HEX0

Table 1: Module `part1` mapping to DE1-SoC pin names

2 Part II

Warning: Please note that this part has a lot of text. Most of it is explanation and guidance, so please **read carefully**.

In this part, you must design an ALU which can be used to calculate equations that involve several additions and multiplications. To do this, you will learn about using **control paths** and **datapaths**, which are used to implement more complex hardware designs.

2.1 Using FSMs in larger designs.

A *finite state machine* (FSM) on its own, like the one built in Part I, cannot do much and is not what you usually do with an FSM except to teach how to build an FSM. The primary use of FSMs is to act as the main control for digital systems that require functions like sequencing or responding in different ways to some stimuli. Part 2 will show you how to use an FSM to do something more interesting than recognizing a pattern of bits.

Control path and Datapath: Most non-trivial digital circuits can be separated into two main functions. One is the *datapath* where the data flows and the other is the *control path* that manipulates the signals in the datapath to control the operations performed and how the data flows through the datapath. In previous labs, you learned how to construct a simple ALU, which is a common datapath component. In Part I of this lab you have already constructed a simple FSM, which is the most common component used to implement a control path. Now you will see how to implement an FSM to control a datapath so that a useful operation is performed. Using an FSM for the control path and an ALU for the datapath is fundamental for how CPUs work. To show you how to write code to implement a control path and a datapath for an ALU, you are provided with code for a sample ALU.

2.2 Sample ALU

For Part 2, you are given a sample ALU that implements an FSM control path and a datapath to compute $A^2 + B$. The same code is provided on the Lab6 page as `part2_template.v`.

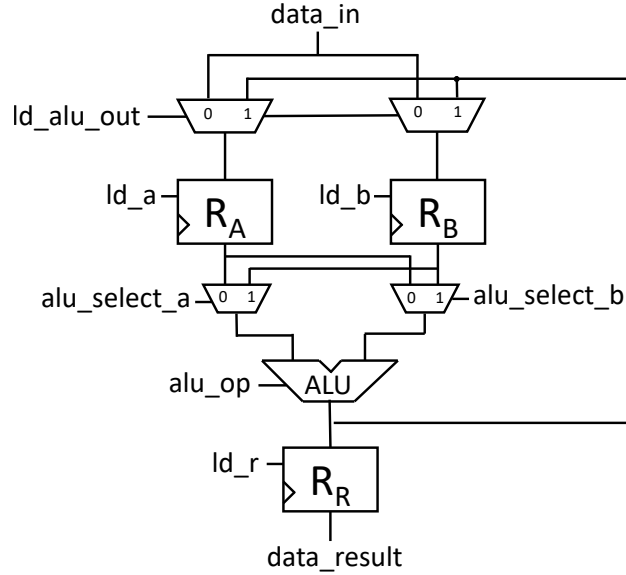


Figure 3: Block diagram of provided datapath.

2.2.1 Datapath

The datapath implemented in the sample code is shown in Figure 3. Study this datapath and the provided code **carefully** to make sure you understand how the code implements the control path and datapath. You must modify this template to implement an expanded datapath for Part 2. As is normal, the clock and reset signals are not shown in Figure 3 to keep the diagram neat, but it is important that you **do not** forget about them. **Reset** is a synchronous active-high reset. Both the provided datapath and the expanded datapath use 8-bit unsigned values. Assume for both cases that the input values are small enough to not cause any overflows at any point in the computation, i.e., no results will exceed $2^8 - 1 = 255$.

There are two registers R_A , R_B used at the start to store the values of A and B , respectively. In a real CPU, these registers may store the result of some previous computation. However, for our datapaths, we load these registers before we start computation. There is one output register, R_R , that captures the output of the ALU. Each of these registers has a load-enable signal, shown with the prefix `ld_` in the Figure. Additionally, the R_A and R_B registers can be overwritten during the computation. This is supported using the 2-to-1 multiplexers controlled by the `ld_alu_out` signal. To select the inputs to the ALU, we use two 8-bit wide, 2-to-1 multiplexers, controlled by the `alu_select_a` and `alu_select_b` signals.

2.2.2 Control path

The provided sample code also implements an FSM for the control path of the ALU. You are **strongly encouraged** to draw the state diagram of this FSM, showing all the inputs and outputs. This will help you to better understand the code and will also serve as a starting point for the FSM you have to write for the expanded ALU.

The FSM first goes through a set of states to load the input registers A and B . We load each register in turn from the `data_in` input when the `Go` signal is asserted. This is implemented in the `S_LOAD` states. However, we cannot be sure that `Go` will only be 1 for a single cycle. This is the case when you run this code on the FPGA and `Go` is connected to a `KEY`. Since the FPGA uses a 50 MHz clock, when you press the `KEY`, many millions of clock cycles will elapse. So if we load A and then B when `Go` is 1, we would load both in the same key press. To avoid this, we need to add a `S_LOAD_WAIT` state for each input. When `Go` becomes 1, we load the input and then go to the `S_LOAD_WAIT` state. There, we wait for `Go` to become 0 before loading the next input. This mimics the user pressing and then releasing the `KEY` input. The computation of $A^2 + B$ occurs in two stages in states `S_CYCLE.0` and `S_CYCLE.1`. When computation is finished, the final result will be loaded into R_R . This final result should be output on port `DataResult` in binary.

The `always@(*)` block labeled `enable_signals` sets the appropriate signals to the datapath for each state in the FSM. Table 2 shows the signals in the control path for each cycle of operation.

Table 2: Register contents and control signals for computing $A^2 + B$

	Reset	1	2	3	4	5	6	7	
Go		1	0	1	0	0	0	0	
data_in		5	5	4	4	-	-	-	- = don't care.
State		0	2	3	4	5	6	1	
R_A		0	5	5	5	5	25	25	
R_B		0	0	0	4	4	4	4	
R_R		0	0	0	0	0	0	29	
ld_a		1	0	0	0	1	0	1	
ld_b		0	0	1	0	0	0	0	
ld_r		0	0	0	0	0	1	0	
ld_alu_out		0	0	0	0	1	0	0	1 = select alu output
alu_select_a		0	0	0	0	0	0	0	0 = select A
alu_select_b		0	0	0	0	0	1	0	1 = select B
alu_op		0	0	0	0	1	0	0	0 = add, 1 = multiply
result_valid		0	0	0	0	0	0	1	

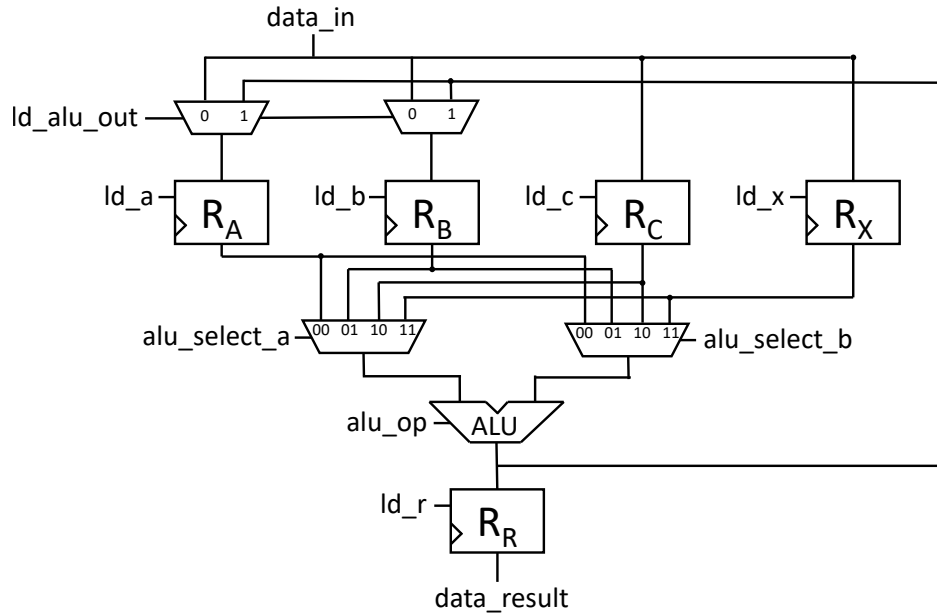


Figure 4: Block diagram of expanded datapath.

You must write a `.do` file to simulate the provided ALU code to understand how it works. Once you are done with this step, you can move on to expanding this ALU to implement a more complex function.

2.3 Expanded ALU

You must modify the provided ALU to implement the equation: $Ax^2 + Bx + C$

Figure 4 shows the block diagram of the datapath you must build. You must change the control and datapath for the provided code to support this expanded ALU. You must modify the code to support four registers: R_A , R_B , R_C and R_X . R_C and R_X are loaded just like R_A and R_B . `Data.in` values should be loaded into registers in the order: R_A , R_B , R_C , R_X . Computation will start after `Go` is set and released for loading R_X . When computation is finished, the final result should be loaded into R_R . This final result should be output on port `DataResult` in binary.

Once the input data is loaded into the appropriate registers, the computation **should not** take more than 7 cycles. When the computation is completed, the `ResultValid` port should be set to 1 at the same cycle that the new valid result is output to `DataResult`. This will indicate to the Automarker (or any downstream block) that the result on the `DataResult` port is ready and valid. `ResultValid` should remain high and `DataResult` should maintain its valid value from the previous computation, indefinitely, until new input is provided, i.e., the `Go` is set to 1. The provided sample ALU already meets the above requirements but you

must make sure your modified ALU does not violate them.

Finally, the ALU only needs to perform addition and multiplication, but you could use a variation of the ALU you built previously to have more operations available for solving other equations if you wish to try some things on your own.

2.4 What to Do

Perform the following steps:

1. Examine the Verilog code provided online in `part2_template.v`. Make a copy called `part2.v`.
2. Prior to coming to lab, create a new table, similar to Table 2 to implement $Ax^2 + Bx + C$. This will inform the new signals you will need in your datapath to support more registers.
3. Prior to coming to lab, add additional states to your FSM State diagram to support loading more registers and performing the additional operations.
4. Modify the control path module to implement the changes to your FSM.
5. Simulate your design by providing 4 values for the registers and checking that your design works.
6. When you are satisfied, you can submit to the automarker.

2.5 Running on the FPGA

To run on the FPGA, use the connections shown in Table 3.

part2 Port Name	Direction	DE1-SoC Pin Name
Reset	Input	KEY[0]
DataIn	Input	SW[7:0]
Go	Input	KEY[1]
DataResult[7:0]	Output	LEDR[7:0] & HEX1, HEX0
ResultValid	Output	LEDR[8]

Table 3: Module `part2` mapping to FPGA pin names

3 Submission

3.1 Part I

For Part I, you need to submit a file named `part2.v` with the following module in it:

```
module part1(Clock, Reset, w, z, CurState);
```

3.2 Part II

For Part II, you need to submit a file named `part2.v` with the following module in it:

```
module part2(Clock, Reset, Go, DataIn, DataResult, ResultValid);
```